



NE-3102: Electronics-II Laboratory

Roll _____ Date _____ Experiment No. _____

Name of the experiment

Implementation of a 4-bit parallel adder using 7483 IC.

Contents

1	Objective	2
2	Theory	2
3	Components and apparatus	4
4	Circuit diagram/setup	4
5	Data collection and analysis	5
6	Result	6
7	Discussion	7
8	References	8

1 Objective

1. To implement a 4-bit parallel adder using 7483 IC.

2 Theory

A parallel adder can be constructed using any number of full adders (FA) by connecting them parallelly. An FA circuit adds two inputs and a carry input and generates one sum and a carry output. One FA's carry output is carry input to the next higher order FA. Thus, all the bits of both augend and addend are tied into the circuit parallelly and addition in each adder always happens simultaneously. For a 4-bit parallel adder, 4 FAs are required. In Figure 2, the variables A_0, A_3, A_2, A_1 , represent the bits of the augend which is stored in the accumulator register, and the variables B_3, B_2, B_1, B_0 represents the bits of the addend which is stored in the B register. variables C_3, C_2, C_1, C_0 represents carry bits into the corresponding FAs. Sum appears at S_3, S_2, S_1, S_0 outputs.

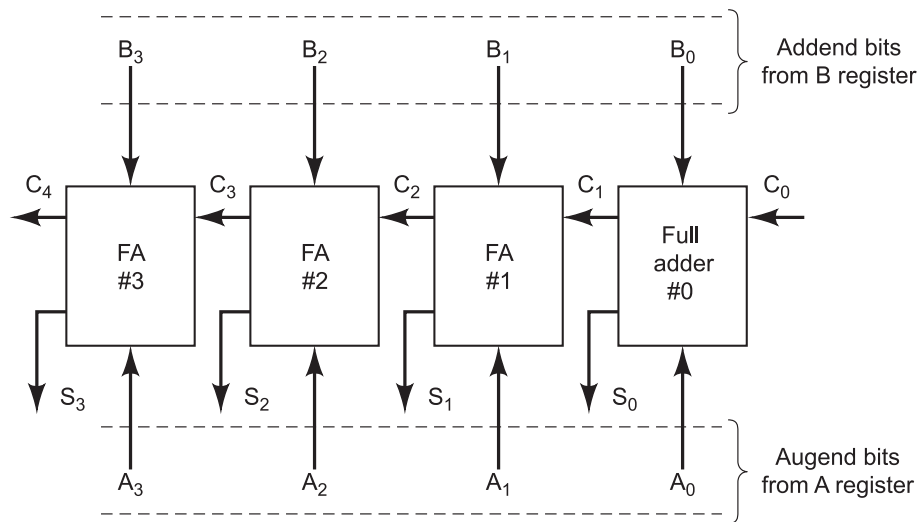


Figure 1: Block diagram of a four-bit parallel adder circuit using full adders.

A				B				Sum				Carry
A_3	A_2	A_1	A_0	B_3	B_2	B_1	B_0	S_3	S_2	S_1	S_0	C_4
0	0	0	0	0	0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1	0	0	1	0	0
0	0	1	0	0	0	1	0	0	1	0	0	0
0	0	1	1	0	0	1	1	0	1	1	0	0
0	1	0	0	0	1	0	0	1	0	0	0	0
0	1	0	1	0	1	0	1	1	0	1	0	0
0	1	1	0	0	1	1	0	1	1	0	0	0
0	1	1	1	0	1	1	1	1	1	1	0	0
1	0	0	0	1	0	0	0	0	0	0	0	1
1	0	0	1	1	0	0	1	0	0	1	0	1
1	0	1	0	1	0	1	0	0	1	0	0	1
1	0	1	1	1	0	1	1	0	1	1	0	1
1	1	0	0	1	1	0	0	1	0	0	0	1
1	1	0	1	1	1	0	1	1	0	1	0	1
1	1	1	0	1	1	1	0	1	1	0	0	1
1	1	1	1	1	1	1	1	1	1	1	0	1
1	1	1	1	1	1	1	1	1	1	1	1	1

Table 1: Truth table for 4-bit parallel adder.

3 Components and apparatus

1. 7483 IC
2. Passive components
3. Breadboard and connecting wires
4. Bench power supply

4 Circuit diagram/setup

The following is the implementation of a four-bit parallel adder circuit:¹

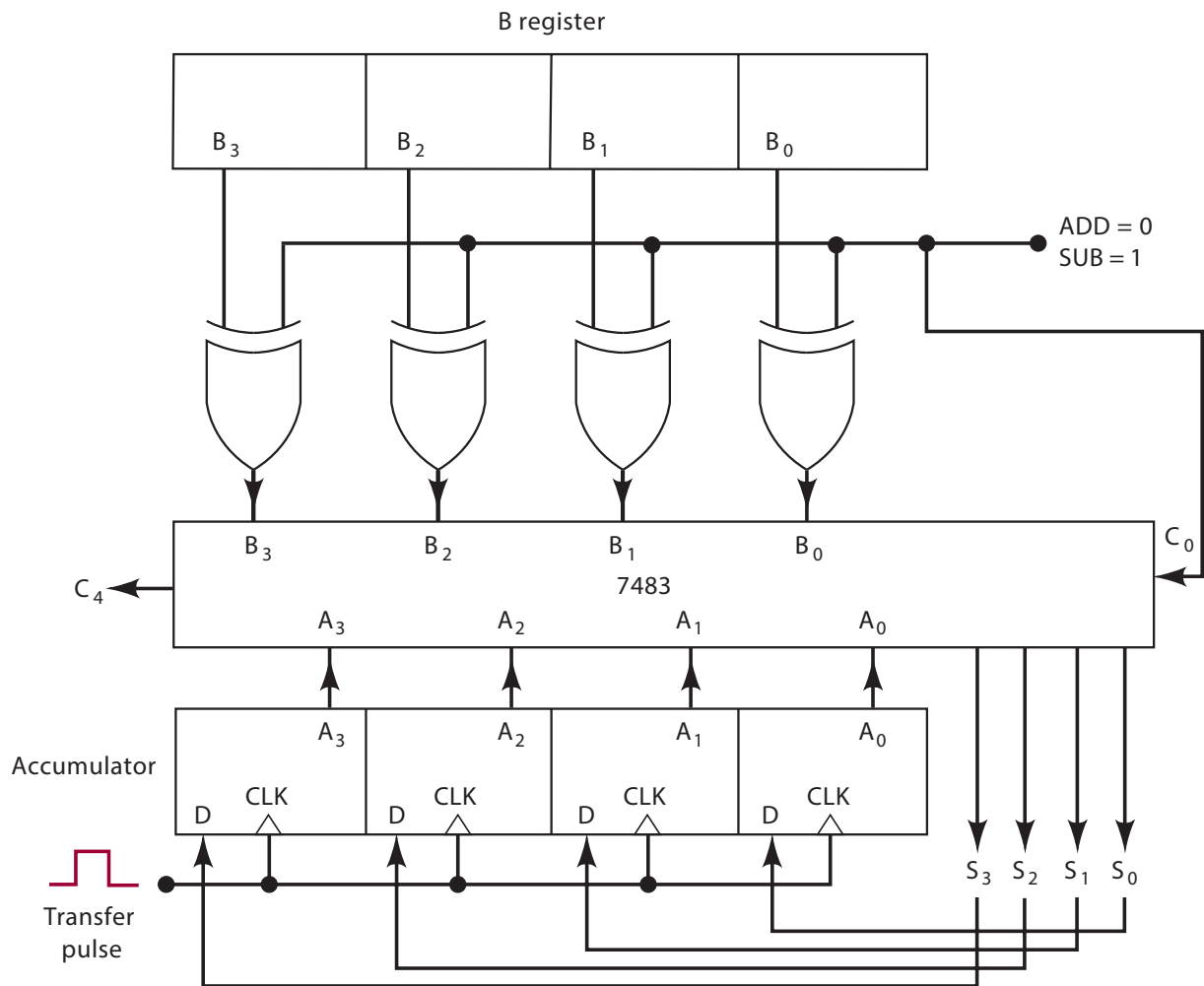


Figure 2: Implementation of a four-bit parallel adder circuit using a 7483 IC.

¹Perform the arithmetic operation $6 + 2 - 4$ (or any other) in the 2's-complement system using the adder. The operation should be done in 2 steps: first perform $6 + 2$ and then perform $8 - 4$. Values in the intermediate and final steps should be stored/accumulated in the Accumulator or the A register. Manually simulate the B register by applying HIGH/LOW on the bits. Use two 7474 D flip-flop ICs for constructing the Accumulator register and asynchronously load the initial augend/minuend: in this case, the value is 6 in 4-bit binary, including the sign bit. Do not put a timing generator/clock; manually synchronize the transfer instead. Note that an array of Ex-OR gates performs the plain binary to 2's-complement conversion between the B register and the points where the values are actually input to the 7483 IC, meaning that you do not need to perform the 2's-complement conversion; the circuit will do that for you. The implementation is essentially a 4-bit arithmetic logic unit (ALU).

5 Data collection and analysis

6 Result

7 Discussion

8 References

1. Tocci Ronald J, Neal W, Greg M. Digital Systems Principles and Applications.

Appendix