



NE-3102: Electronics-II Laboratory

Roll _____ Date _____ Experiment No. _____

Name of the experiment

Truth table verification of S-R, T, D, J-K flip-flop.

Contents

1 Objective	2
2 Theory	2
2.1 S-R latch	2
2.2 S-R flip-flop	2
2.3 Conversion of S-R flip-flop to D flip-flop	3
2.4 Conversion of S-R flip-flop to J-K flip-flop	3
2.5 Conversion of S-R flip-flop to T flip-flop	3
2.6 Timing generator/clock	3
3 Components and apparatus	6
4 Circuit diagram/setup	7
5 Data collection and analysis	8
6 Result	9
7 Discussion	10
8 References	11

1 Objective

1. To implement a S-R latch using NAND/NOR¹ gates.
2. To design and implement a generic astable multivibrator with 0.2 Hz and 50% duty cycle square wave output as a timing generator/clock²
3. To implement a S-R flip-flop based on a S-R NAND/NOR latch
4. To convert the S-R flip-flop to a D flip-flop
5. To convert the S-R flip-flop to a J-K flip-flop
6. To convert the J-K flip-flop to a T flip-flop
7. To verify the associated function tables

2 Theory

A latch or a flip-flop is an electric circuit with two stable states that can store binary data. This stored data can be changed by applying one or more inputs. Latches and flip-flops are fundamental building blocks of logic circuits that incorporate memory cells; their output depends on the present value of the input and also on the previous values. These circuits, also called sequential logic circuits, often require a timing generator (a clock) for their operation. Usually there are two outputs, Q and its complementary value \bar{Q} .

2.1 S-R latch

(description)

 


Figure 1: S-R latch.

2.2 S-R flip-flop

(description)

¹Either use NAND or NOR gates; this will affect your input/output active states, e.g., a NAND S-R latch will have active LOW inputs, so you have to pull your inputs HIGH with pull-up resistors for the resting state

²The implementation of the timing generator/clock can be based on a 555 timer IC/Schmitt trigger oscillator/crystal oscillator/microcontroller

 


Figure 2: S-R flip-flop.

2.3 Conversion of S-R flip-flop to D flip-flop

(description)

 


Figure 3: D flip-flop.

2.4 Conversion of S-R flip-flop to J-K flip-flop

(description)

2.5 Conversion of S-R flip-flop to T flip-flop

(description)

2.6 Timing generator/clock

555 timer is made up of two voltage comparators and an S-R latch as shown in Figure 6. The voltage comparators are devices that produce a HIGH out whenever the voltage on the + input is greater than the voltage on the - input. The external capacitor (C) charges up until its voltage exceeds $2/3 \times V_{CC}$ as determined by the upper voltage comparator monitoring V_{T+} . When this comparator output goes HIGH, it resets the SR latch, causing the output pin (3) to go LOW. At the same time, \bar{Q} goes HIGH, closing the discharge switch and causing the capacitor to begin to

 


Figure 4: J-K flip-flop.

 


Figure 5: T flip-flop.

discharge through R_B . It will continue to discharge until the capacitor voltage drops below $\frac{1}{3} \times V_{CC}$ as determined by the lower-voltage comparator monitoring V_{T-} . When this comparator output goes HIGH, it sets the S-R latch, causing the output pin to go HIGH, opening the discharge switch and allowing the capacitor to start charging again as the cycle repeats.

The formulas for these time intervals, t_L and t_H , and the overall period of the oscillations, T , are given in the figure. The frequency of the oscillations is, of course, the reciprocal of T . As the formulas in the diagram indicate, the t_L and t_H intervals cannot be equal unless R_A is made zero. This cannot be done without producing excess current through the device. This means that it is impossible to produce a perfect 50 percent duty-cycle square wave output with this circuit. It is possible, however, to get very close to a 50 percent duty cycle by making $R_B \gg R_A$ (while keeping R_A greater than $1k\Omega$), so that $t_L \approx t_H$.

 


Figure 6: 555 astable multivibrator.

3 Components and apparatus

1. Logic³ ICs
2. 555 timer IC
3. Passive components
4. Breadboard and connecting wires
5. Bench power supply

³Specify exactly what ICs you are using in your build

4 Circuit diagram/setup

5 Data collection and analysis

S	R	Q
0	0	Q_0 (no change)
1	0	1
0	1	0
1	1	(ambiguous)

Table 1: Function table for S-R latch.

S	R	CLK	Q
0	0	\uparrow	Q_0 (no change)
1	0	\uparrow	1
0	1	\uparrow	0
1	1	\uparrow	(ambiguous)

Table 2: Function table for S-R flip-flop with active low inputs and PGT triggering.

T	CLK	Q
0	\uparrow	Q_0 (no change)
1	\uparrow	$\overline{Q_0}$ (toggle)
1	\uparrow	1

Table 3: Function table for T flip-flop with active low inputs and PGT triggering.

D	CLK	Q
0	\uparrow	0
1	\uparrow	1

Table 4: Function table for D flip-flop with active low inputs and PGT triggering.

J	K	CLK	Q
0	0	\uparrow	Q_0 (no change)
1	0	\uparrow	1
0	1	\uparrow	0
1	1	\uparrow	$\overline{Q_0}$ (toggle)

Table 5: Function table for J-K flip-flop with active low inputs and PGT triggering.

6 Result

7 Discussion

(You are expected to elaborate on possible timing implications and reflect on your setup-specific details e.g., the choice of NAND/NOR gates, active states on the input(s) and outputs, and so on.)

8 References

1. Tocci Ronald J, Neal W, Greg M. Digital Systems Principles and Applications.

Appendix